

The voltage across the cell (A) is 1.5V. The voltage across lamp B is 1.5V. What is the voltage across lamp C?