

The voltage across the cell (A) is 9V. What is the voltage across lamp C?