



The voltage across the lamp is 2V. The current through the lamp is 1A. How much electrical power is the lamp using, in watts?