



The current at point D is 2A. What is the current at point A?