

What is the total resistance of a series circuit containing a 10 ohm and a 5 ohm resistor?