

The current through lamp B is 0.5A. The current through lamp C is 1A. What is the current at point A?