



The voltage decrease across the lamp (B) is 1.5V . What is the voltage increase across the cell (A)?