



The voltage increase across the cell (A) is 6V. What is the voltage increase across the lamp (B)?