

When an extra lamp is added to a series circuit, the
.....