

What is the total resistance of a series circuit which has two 10 ohm resistors?