

If we add an extra lamp to a series circuit, what will happen to the current?