



The voltage decrease across the lamp (B) is  $1.2\text{V}$ . What is the voltage increase across the cell (A)?