



The current at point A is 1.5A. What is the current at point D?