

Should an ammeter be connected in series or parallel?