

The current at point A is 0.5A. The current through lamp B is 0.1A. What is the current through lamp C, in amps?