



The voltage across the cell (A) is 12V. What is the voltage across lamp C?