



The current through lamp B is 2A. The current through lamp C is 1A. What is the current at point D?