



The current through lamp B is  $0.5\text{A}$ . The current through lamp C is  $1\text{A}$ . What is the current at point A?