



The voltage across the lamp is 3V. The resistance of the lamp is  $1.5\Omega$ . What is the current through the lamp?