



The voltage across the lamp is 3V. The resistance of the lamp is 1.5Ω . What is the current through the lamp?