



The voltage across the lamp is 3V. The current through the lamp is 1.5A. How much electrical power is the lamp using, in watts?