



The voltage across the lamp is 1 V . The resistance of the lamp is 4Ω . What is the current through the lamp?