



The current through the ammeter is 5A. The voltage across the lamp is 10V. What is the resistance of the lamp, in ohms?