



The voltage across the cell (A) is  $1.5\text{V}$ . The voltage across lamp B is  $1.5\text{V}$ . What is the voltage across lamp C?