



The current through the ammeter is 4A. The resistance of the lamp is  $20\Omega$ . What is the voltage across the lamp?