



The current through the ammeter is 1A. The voltage across the lamp is 1V. What is the resistance of the lamp, in ohms?