



The current through the ammeter is 1A. The resistance of the lamp is 30. What is the voltage across the lamp?