



The current through the ammeter is 0.5A . The resistance of the lamp is 3Ω . What is the voltage across the lamp?