



The voltage increase across the cell (A) is 12V. What is the voltage decrease across the lamp (B)?