A circuit that has two or more paths for electricity to flow is called a .... circuit.